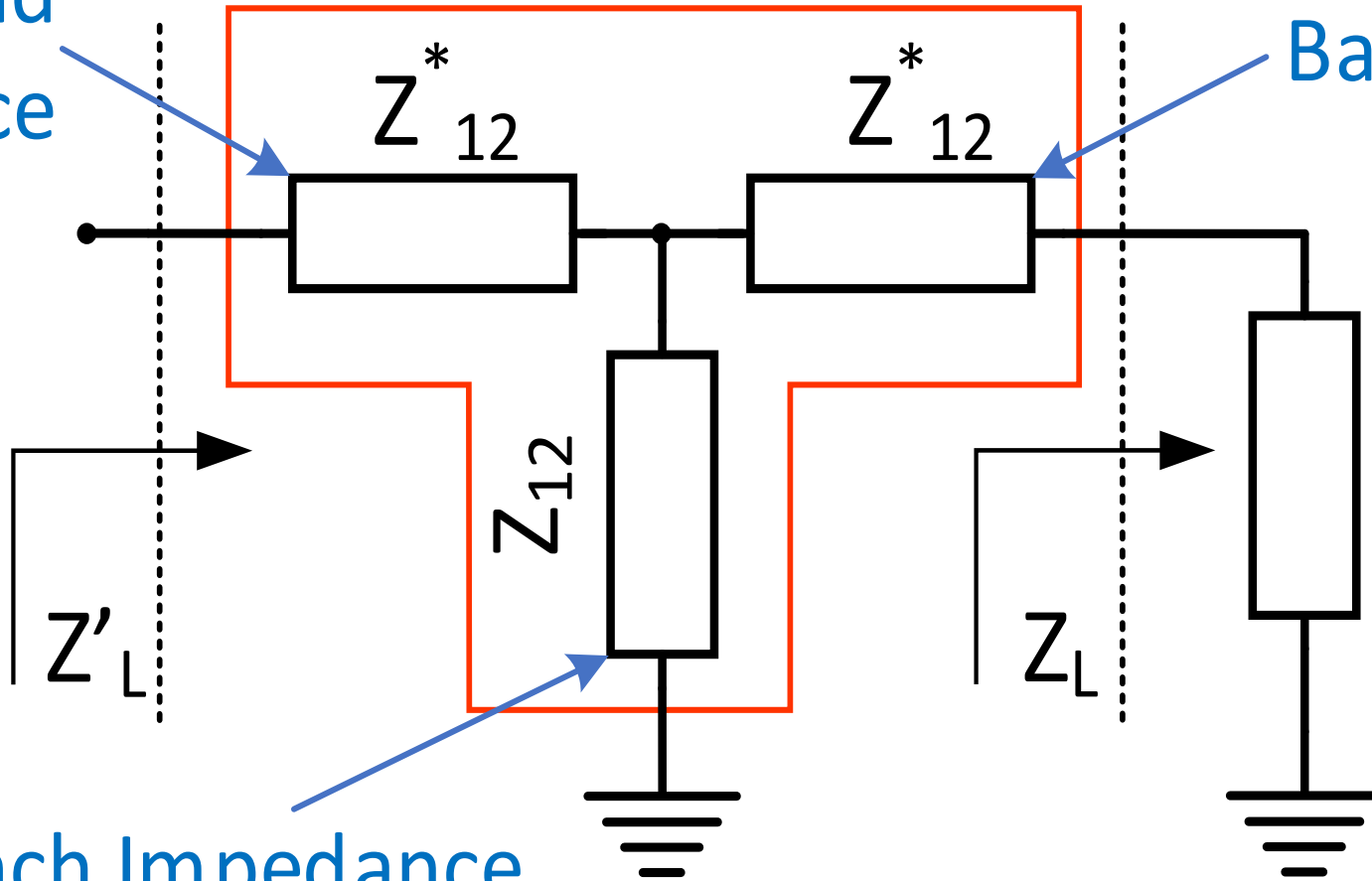


Symmetric T-Bridge

Front-end Impedance

Back-end Impedance

Mid-branch Impedance



Capacitive Coupling:

$$Z_{12} = -jX_C$$

Inductive Coupling:

$$Z_{12} = +jX_L$$